
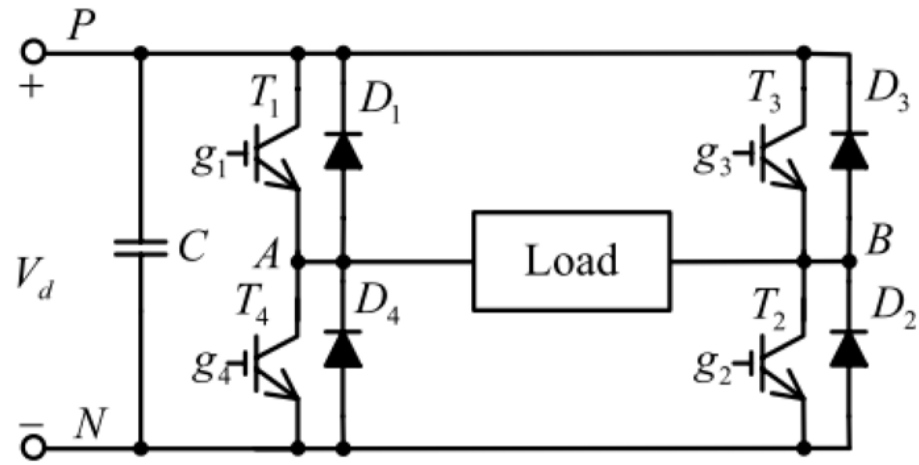


Single Phase Full Bridge with PWM operation

• Waveforms, bipolar PWM

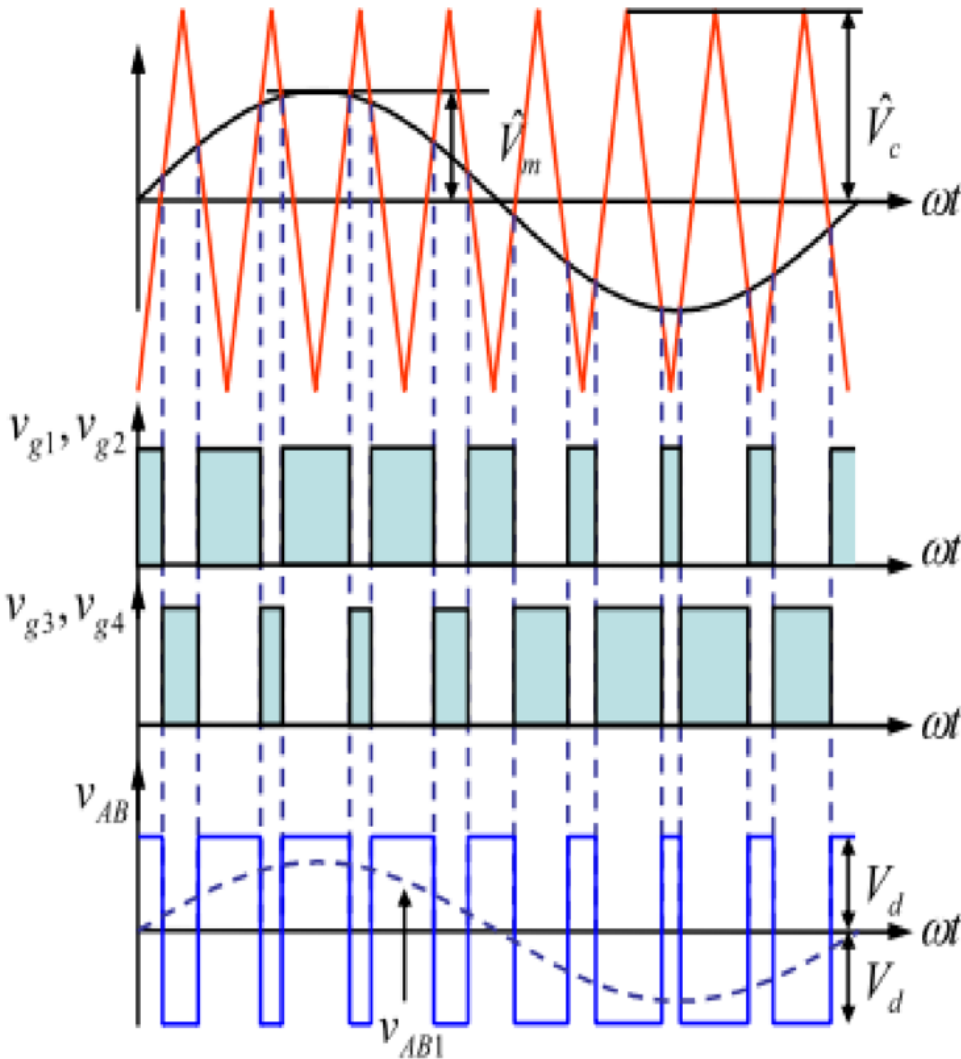

(1) v_{g1} and v_{g4} are complimentary signals

v_{g2} and v_{g3} are complimentary signals

(2) $v_m \geq v_c \rightarrow v_{g1} = v_{g2} = \text{logic "1"}$

$v_m < v_c \rightarrow v_{g1} = v_{g2} = \text{logic "0"}$

(3) When $v_{g1} = v_{g2} = \text{logic "1"} \rightarrow T_1$ and T_2 on $\rightarrow v_{AB} = V_d$

When $v_{g1} = v_{g2} = \text{logic "0"} \rightarrow T_3$ and T_4 on $\rightarrow v_{AB} = -V_d$